



CSE4117 MICROPROCESSORS
ASSIGNMENT #4 Report

150119679 - Muhammedcan PİRİNÇÇİ

150117061 - İsra Nur ALPEREN


150116836 - Enes Nadir SANLI

❖ Overview of the Project


In this assignment we added some new modules and using all the previous modules we completed the given work. But to be able to apply previous components to this work we would make some modifications on them. We increased the total instruction bit for one value and this value keeps the information of whether the instruction is L-type or R-type. Some new signals inside the control unit “MA, WD, RD”. New modules are rom, program counter, and register controller. We used a register controller module three times and those are taking the input signal of MA, WD, and RD.

For the program counter simulation we wrote basic instructions to see if every module works fine. In this example we use instructions that write, read to ram(R - type) and also classic L type.

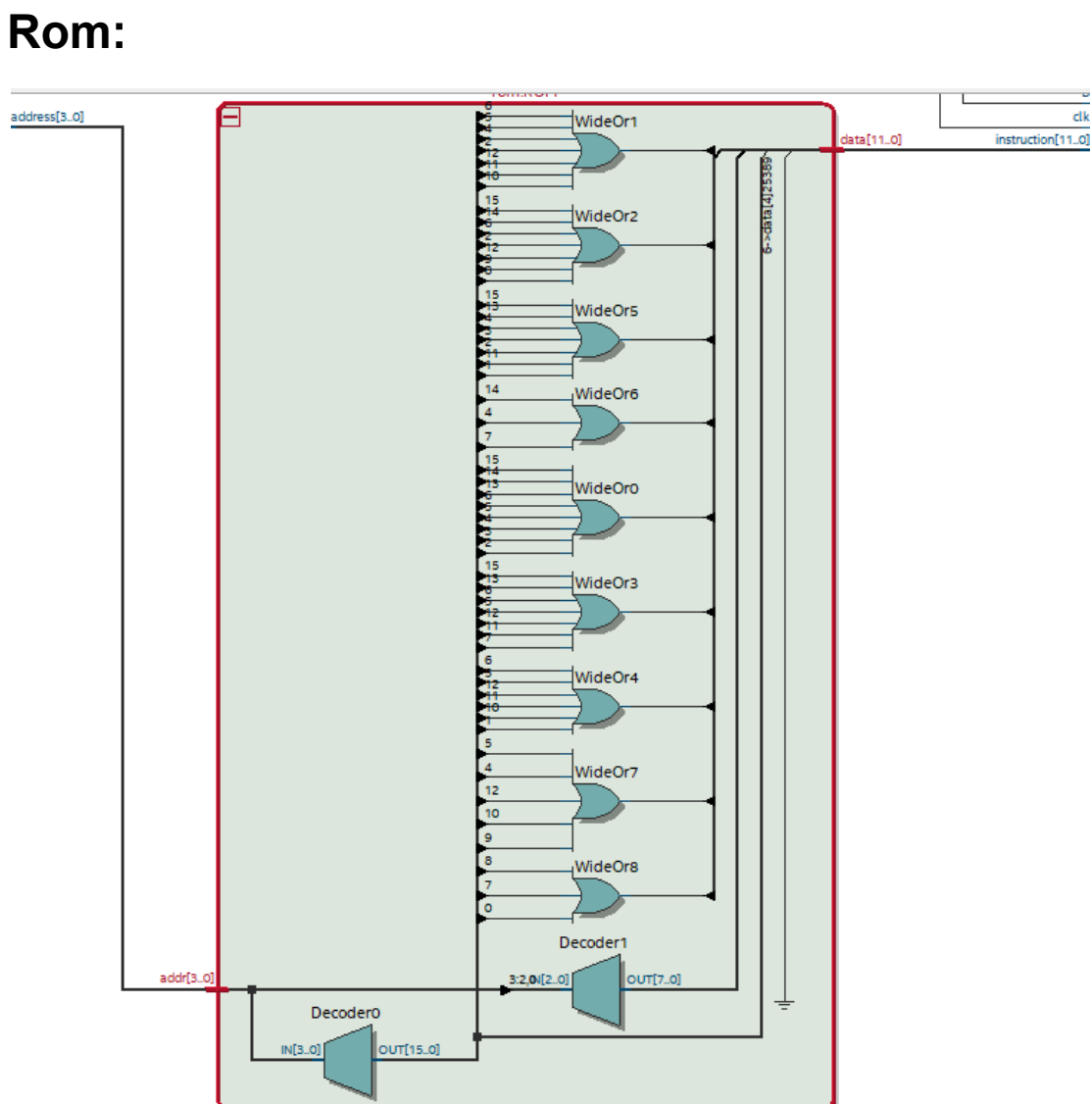
```
4'b0000 : data = 12'b0000000000001; // 0 # add, 1 -> acc = 1
4'b0001 : data = 12'b000001100000; // 1 # add, 01100000 -> acc =
01100001
4'b0010 : data = 12'b111000100000; // 2 # storer, 100000 ->
addr[100000] = 01100001
4'b0011 : data = 12'b100000100000; // 3 # addr, 100000 -> acc =
(01100001 + 01100001) = 11000010
```




Register Controller:

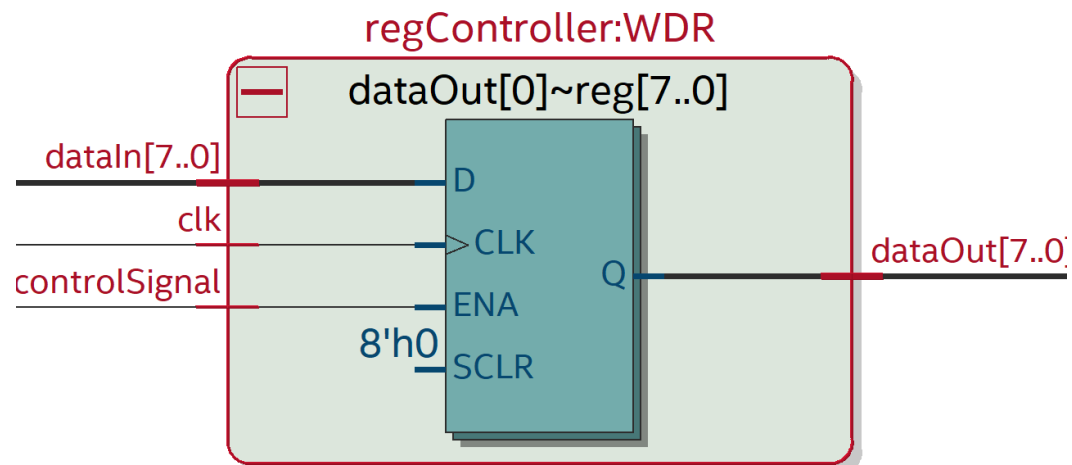


Instruction Register:

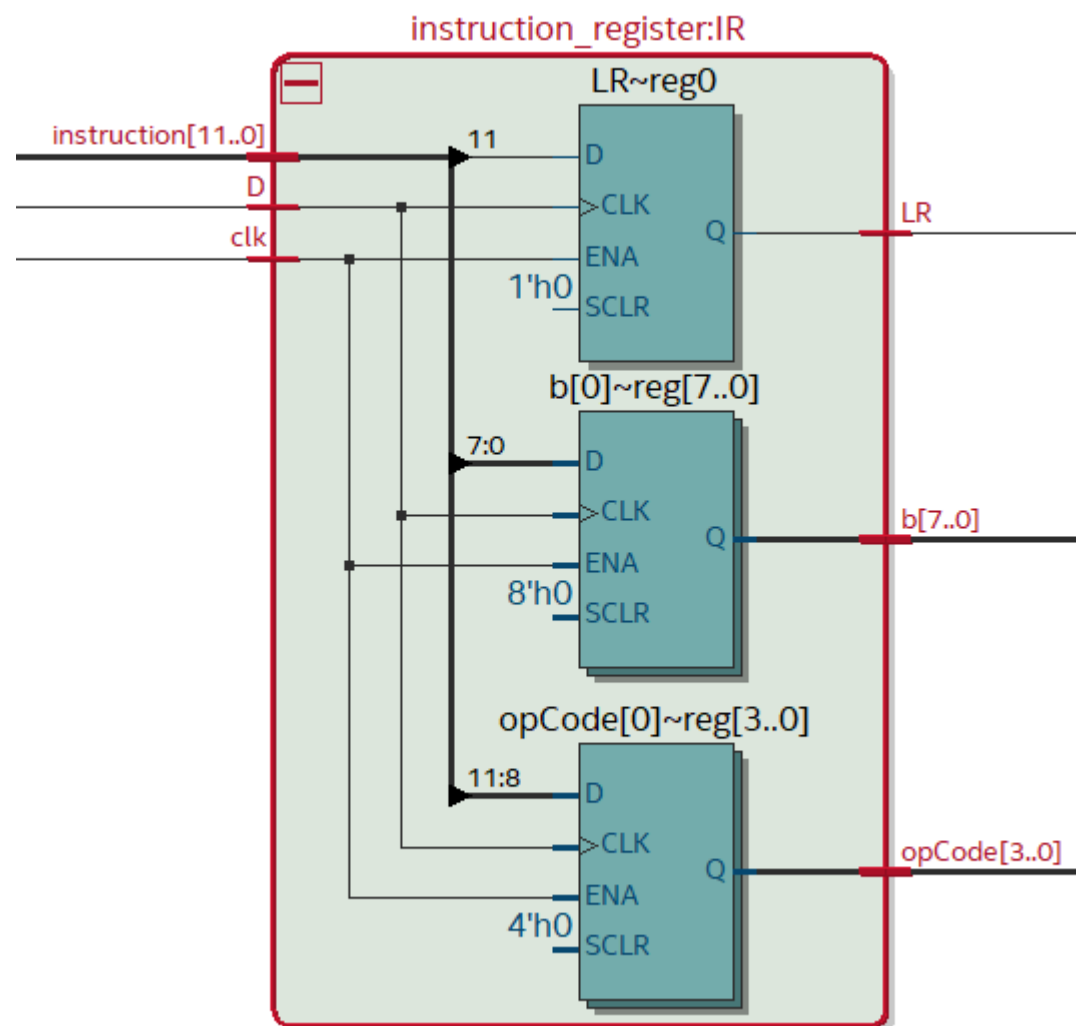

Control Unit:

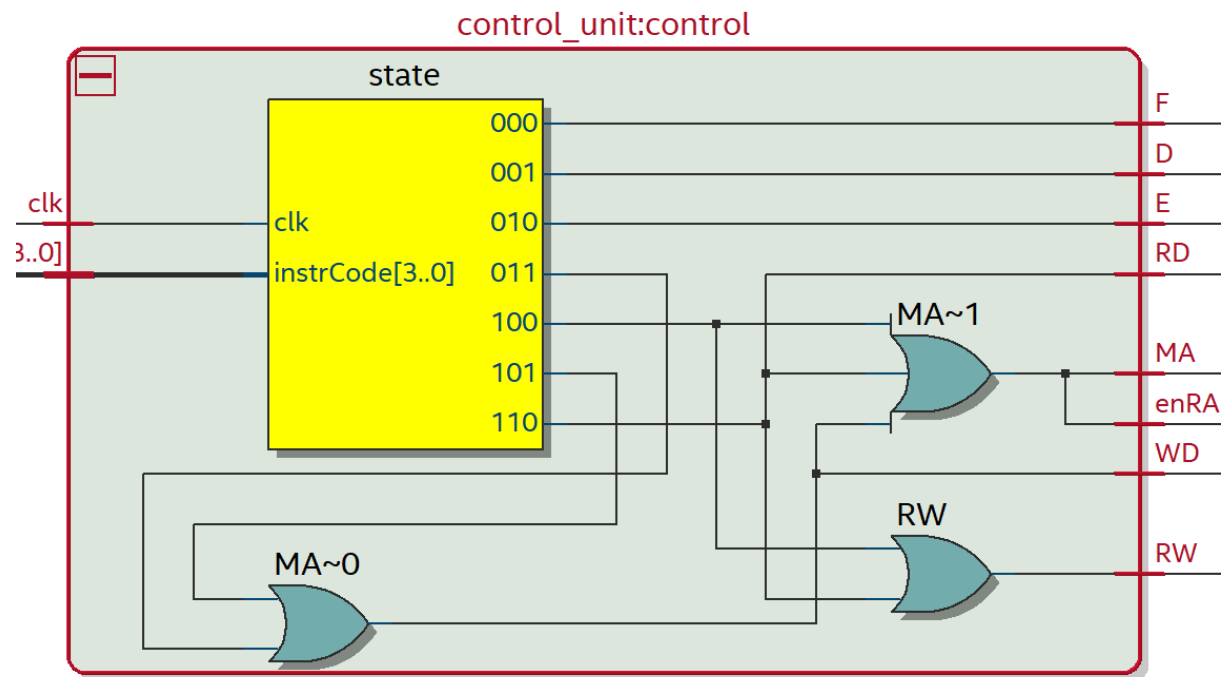


Assignment 4:

 

Test Results:

 We made our simulation on the ModelSim simulation tool.
The results were as we expected.



❖ New Verilog Files

counter.v file:

```
module counter( clk, F, address);  
input clk, F;  
output reg [3:0] address;  
  
initial address = 4'b1111;  
  
always@(posedge F)  
begin  
address = address + 1;  
end  
  
endmodule
```

rom.v file:

```
module rom(addr,data);
input [3:0] addr;
output reg [11:0] data;

always@ (*)
begin
    case(addr)
        4'b0000 : data = 12'b000000000001; // 0
        4'b0001 : data = 12'b000001100000; // 1
        4'b0010 : data = 12'b111000100000; // 2
        4'b0011 : data = 12'b100000100000; // 3
        4'b0100 : data = 12'b110000101100; // 4
        4'b0101 : data = 12'b110101000100; // 5
        4'b0110 : data = 12'b111101010000; // 6
        4'b0111 : data = 12'b000100001001; // 7
        4'b1000 : data = 12'b001000000001; // 8
        4'b1001 : data = 12'b001000000100; // 9
        4'b1010 : data = 12'b010001000100; // a
        4'b1011 : data = 12'b010101100000; // b
        4'b1100 : data = 12'b011111000100; // c
        4'b1101 : data = 12'b100100100000; // d
        4'b1110 : data = 12'b101010001000; // e
        default : data = 12'b101100100000; // f
    endcase
end
endmodule
```

regController.v file:

```
module regController(clk, controlSignal, dataIn, dataOut);
input clk, controlSignal;
input [7:0] dataIn;
output reg [7:0] dataOut;
initial dataOut = 8'b0;

always@(*)
begin
    dataOut = ( clk ==1 & controlSignal==1) ? dataIn: dataOut;
end
endmodule
```

assignment4.v file:

```
module assignment4(clk);
input clk;
wire[7:0] addrLiteral, acIn, acOut, dataB, RDR_Out, WDR_Out, MAR_Out, RAM_Out ;
wire[3:0] opCode;
wire[11:0] instruction;
wire MA, WD, RD, enRAM, RW, LR, F, D, E, zFlag, nFlag, cFlag, ofFlag;
wire[3:0] nextInstrAdd;

instruction_register IR(clk, instruction, D, opCode, addrLiteral, LR);
control_unit control(clk,opCode, F , D, E, MA, WD, RD, enRAM, RW);
counter PC( clk, F, nextInstrAdd);
rom ROM(nextInstrAdd,instruction);
ram RAM(RAM_Out, WDR_Out, MAR_Out,enRAM, RW);
regController MAR(clk, MA, addrLiteral, MAR_Out);
regController WDR(clk, WD, acOut, WDR_Out);
regController RDR(clk, RD, RAM_Out, RDR_Out);
assign dataB = LR ? RDR_Out: addrLiteral;////////////////////////////////////

alu8 alu( acIn, dataB, acOut, zFlag, nFlag, cFlag, ofFlag, opCode );
acc Acc(clk, acIn, (E | RW) , acOut);

endmodule
```

control_unit.v file:

```
module control_unit(Clk, InstrCode, F, D, E, MA, WD, RD, enRAM, RW);
input Clk;
input [3:0] InstrCode;
output F, D, E, MA, WD, RD, enRAM, RW;
reg [2:0] state;

initial state = 3'b000;
always @(posedge Clk)
begin
    if((Clk == 1) && (state == 3'b000)) // F state to D state
        state = 3'b001; // D state

    // L type
    else if((state == 3'b001) && ~InstrCode[3]) // D state to E
        state = 3'b010; // E state - alu

    else if(state == 3'b010) // E state to F state
        state = 3'b000; // F state

    // Write
    else if((state == 3'b001) & InstrCode[3] & (InstrCode[2] & InstrCode[1] & ~InstrCode[0])) // D state to WR - storer (if we use fsr we have to add it)
        state = 3'b011; // WR state

    else if(state == 3'b011) // WR to Execute store state
        state = 3'b101; // Execute store state

    else if(state == 3'b101) // Execute store state to
        state = 3'b000; // F state

    // Read Ram
    else if((state == 3'b001) && InstrCode[3]) // D state to RR
        state = 3'b100; // RR

    else if(state == 3'b100) // RR to Execute load state
        state = 3'b110; // Execute store state

    else if(state == 3'b110) // Execute store state to F state
        state = 3'b000; // F state
end

L
assign F = (state == 3'b000) ? 1 : 0;
assign D = (state == 3'b001) ? 1 : 0;
assign E = (state == 3'b010) ? 1 : 0;
assign RD = (state == 3'b110) ? 1 : 0;
assign RW = ((state == 3'b100) || (state == 3'b110)) ? 1 : 0;
assign WD = ((state == 3'b011) || (state == 3'b101)) ? 1 : 0;
assign enRAM = ((state == 3'b011) || (state == 3'b101) || (state == 3'b100) || (state == 3'b110)) ? 1 : 0;
assign MA = ((state == 3'b011) || (state == 3'b101) || (state == 3'b100) || (state == 3'b110)) ? 1 : 0;

endmodule
```